



Higher Physics Homework Tutorials

# Unit 2

Electricity & Electronics

Version 2.0


Solutions

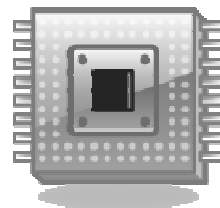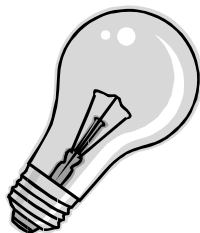


## Tutorial 1 Charges & Electric Fields

1. Draw a diagram showing the electric field in each of the following:


(a)

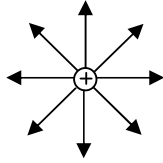

(b)

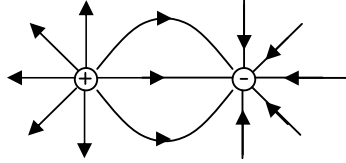

(c)

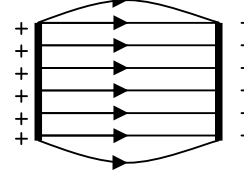

2. Calculate the work done on a proton which is placed in a 3kV electric field.

$$E_w = QV = 1.6 \times 10^{19} \times 3000 = 4.8 \times 10^{-16} \text{ J}$$

3. In a particle accelerator, electric fields are used to accelerate sub atomic particles. By equating work done and kinetic energy, find the velocity of each of the following when placed in a 14kV electric field, assuming the particles are initially at rest.

(a)  $1.6 \times 10^6 \text{ ms}^{-1}$

(b)  $7.0 \times 10^7 \text{ ms}^{-1}$

(c)  $1.2 \times 10^6 \text{ ms}^{-1}$

4. Calculate the voltage of electric field required to accelerate an electron from rest to 6% of the speed of light in a vacuum.

922 V

5. Two opposite charged plates are set up as shown and a proton is fired into the field from the left through a small hole in the plate at a velocity of  $8 \times 10^6 \text{ ms}^{-1}$ . The electric field has a voltage of 6kV. Calculate


(a)  $E_w = QV = 9.6 \times 10^{-16} \text{ J}$

(b)  $E_k = \frac{1}{2}mv^2 = 5.35 \times 10^{-14} \text{ J}$

(c) Initial  $E_k + E_w = 5.45 \times 10^{-14} \text{ J}$

(d)  $8.1 \times 10^6 \text{ ms}^{-1}$

(e)  $7.37 \times 10^{-16} \text{ N}$

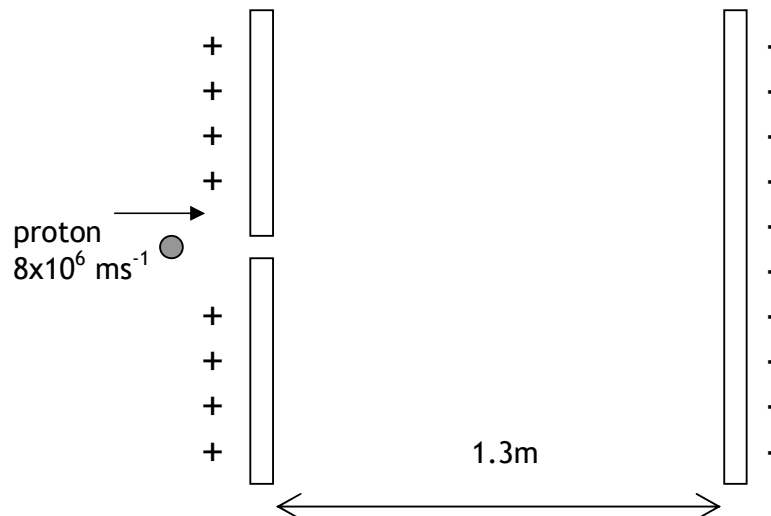

## Tutorial 2

### Circuits Revision

1. Calculate the total resistance of each of the following combinations of resistors if each resistor has a resistance of  $15\Omega$ :

- (a)  $R_T = 15 + 15 = 30\ \Omega$
- (b)  $R_T = 15/3 = 5\ \Omega$
- (c)  $R_T = 15 + (15/2) = 22.5\ \Omega$
- (d)  $R_T = (15/2) + (15/2) = 15\ \Omega$

2. Calculate the unknown readings on the voltmeter and ammeter in each circuit:


- (a)  $R_p = 7.2\ \Omega$  ,  $R_t = 13.2\ \Omega$  , Ammeter reading =  $1.82\ \text{A}$   
Voltmeter reading =  $IR = 10.9\ \text{V}$
- (b)  $R_t = 70.91\ \Omega$  , Ammeter reading =  $0.085\ \text{A}$   
Voltmeter reading = voltage divider =  $1.54\ \text{V}$

3. Calculate the current drawn by and resistance of the following mains (230V) appliances:

- (a)  $0.017\ \text{A}$
- (b)  $13.04\ \text{A}$

4. Calculate the current drawn from the supply in the circuit below when

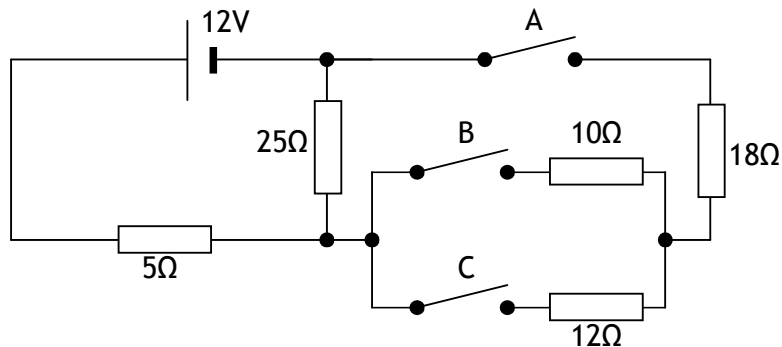- (a)  $R_t = 25 + 5 = 30\ \Omega$  ,  $I = 0.4\ \text{A}$
- (b)  $(18 + 12)\Omega$  in parallel with  $25\ \Omega$   $R_t = 5 + 13.64 = 18.64\ \Omega$  ,  $I = 0.64\ \text{A}$
- (c)  $(10 + 12$  in par =  $5.45\ \Omega) + 18 = 23.45\ \Omega$   
 $(23.45$  in par with  $25) + 5$   $R_t = 17.1\ \Omega$  ,  $I = 0.70\ \text{A}$



## Tutorial 3 Internal Resistance

1. State what is meant by each of the following
  - (a) energy given to each coulomb of charge
  - (b) a resistance caused by the chemicals in the cell results in terminal voltage drop
  - (c) difference between the emf and tpd, voltage across internal resistance
  - (d) the measured voltage across the terminals of the cell
  
2. A battery is tested under open circuit conditions with a voltmeter and produces a voltage of 13V. When connected to a  $5\Omega$  load resistor, the voltage drops to 12.3V.
  - (a) 13V
  - (b)  $r=0.28\ \Omega$
  
3. An AA cell has an emf of 1.5V and an internal resistance of  $1.3\Omega$ . Calculate the following:
  - (a)  $I_{sc}=1.15\ \text{A}$
  - (b)  $V_{tpd}=1.13\ \text{V}$
  - (c)  $I=0.35\ \text{A}$
  - (d)  $I=0.22\ \text{A}$
  
4. A battery has an emf of 12V and an internal resistance of  $2\Omega$ .
  - (a)  $P = 14.7\ \text{W}$
  - (b)  $P = 17.8\ \text{W}$
  
5. Describe in detail an experiment to measure the internal resistance of a cell. Include a circuit diagram, a note of all measurements you would take and a description of any calculations you would perform.

*There are a couple of options but basically*  
*Measure emf by connecting a voltmeter to the cell - no current flowing*  
*Connect external resistor of known resistance, measure current and tpd*  
*Use these in  $E=V_{tpd}+Ir$*
  
6. Two cells are available. Cell A has an emf of 3V and an internal resistance of  $0.6\Omega$ , while cell B has an emf of 5V and an internal resistance of  $2.3\Omega$ . Show by calculation which of the two cells will produce the greatest power output when connected to a  $3\Omega$  heating element.

Cell A -  $P=2.08\ \text{W}$   
Cell B -  $P=2.66\ \text{W}$

Tutorial 4  
Voltage dividers & Wheatstone Bridges

1. *In each of the following voltage divider circuits find the voltage across the larger resistor.*

(a) 20V

(b) 7.4V

(c) 16V

2. *In each of the following Wheatstone bridge circuits, calculate the value of the missing resistor in order to make the reading on the voltmeter zero.*

(a) 106.7  $\Omega$

(b) 150  $\Omega$

(c) 161  $\Omega$

3. *By considering the circuits below as two potential dividers, calculate the potential difference across the Wheatstone bridge (the reading on the voltmeter).*

(a) 0.69 V

(b) 0.33V


(c) 0.75V

## Tutorial 5 AC and DC Voltages & Currents


1. The following voltages are all given as peak voltages. Calculate the rms equivalent for each:

- (a)  $230 \text{ V}_{\text{peak}} = 162.6 \text{ V}_{\text{rms}}$
- (b)  $11,000 \text{ V}_{\text{peak}} = 7778 \text{ V}_{\text{rms}}$
- (c)  $50 \text{ V}_{\text{peak}} = 35.3 \text{ V}_{\text{rms}}$

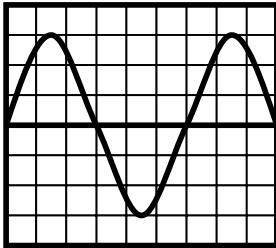
2. Using the view on the oscilloscopes shown and the settings noted below each, state the peak value of the voltage and its period, and therefore calculate its frequency.



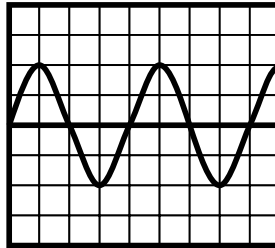Time base = 5 ms/div  
 V Gain = 0.2 V/div  
 $V_{\text{peak}} = 0.6 \text{ V}$   
 Period = 30ms  
 $f = 33 \text{ Hz}$



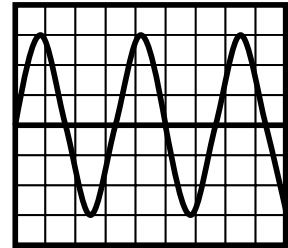
Time base = 50  $\mu\text{s}$ /div  
 V Gain = 0.01 V/div  
 $V_{\text{peak}} = 0.02 \text{ V}$   
 Period = 200  $\mu\text{s}$   
 $f = 5000 \text{ Hz}$



Time base = 0.5 s/div  
 V Gain = 2 V/div  
 $V_{\text{peak}} = 6 \text{ V}$   
 Period = 1.67 s  
 $f = 0.6 \text{ Hz}$

3. The following circuit is supplied with an AC supply which has a peak voltage of 400V. Calculate:

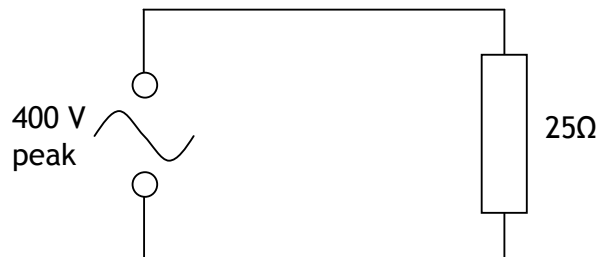- (a)  $V_{\text{rms}} = 282.8 \text{ V}$
- (b)  $I_{\text{rms}} = 11.3 \text{ A}$
- (c)  $I_{\text{peak}} = 16 \text{ A}$
- (d)  $P = 3192 \text{ W}$




## Tutorial 6 Capacitors

1. A  $500\mu\text{F}$  capacitor is charged from a DC supply. Calculate the charge stored on the capacitor when it is charged to:

- (a) 1 mC
- (b) 3 mC
- (c) 0.012 C

2. The circuit below is set up to analyse the charging and discharging behaviour of a  $0.3\text{mF}$  capacitor. With the two way switch in position 1, the capacitor is allowed to become fully charged. When the switch is moved to position two, the capacitor discharges through the  $3\Omega$  load resistor. Calculate:

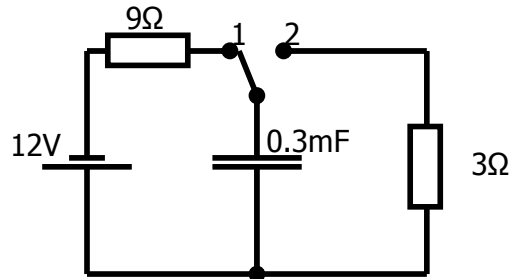- (a)  $I = 1.33\text{ A}$
- (b) Fully charged current = 0 A
- (c)  $E = 0.036\text{ J}$
- (d)  $Q = 3 \times 10^{-3}\text{ C}$
- (e)  $I = 4\text{ A}$



3. A similar charging and discharging circuit to that used in Q2 is used to measure how the voltage across the capacitor and current through it vary with time.

The voltage supply is activated at time=0 with the capacitor completely discharged. The capacitor becomes fully charged after 6 seconds.




7s from the start of charging, the switch is moved to position 2 and the capacitor fully discharges in 3 seconds.

Calculate numerical values for the voltage and current at  $t=0$ ,  $t=6$ ,  $t=7$  and  $t=10\text{s}$ .

Use these values to sketch a graph with numerical values on both axes for

- (a) the voltage across the capacitor against time
- (b) the current through the capacitor against time

	(a)		(b)	
$t=0$	-	0	-	1.5A
$t=6$	-	12V	-	0A
$t=7$	-	12V	-	-3A
$t=10$	-	0V	-	0A

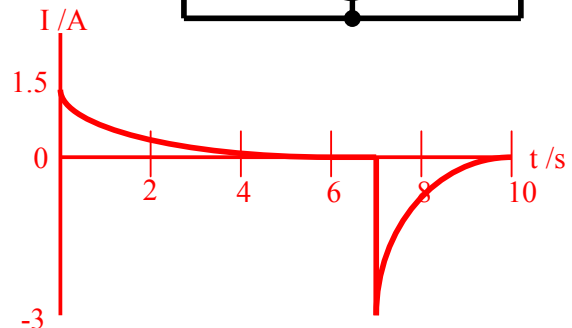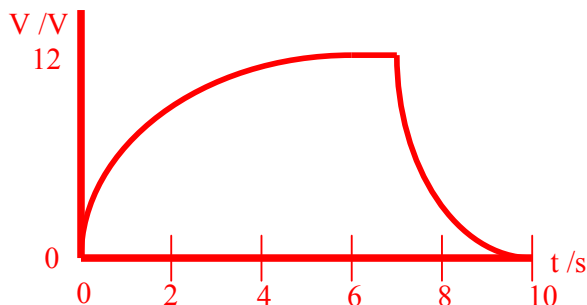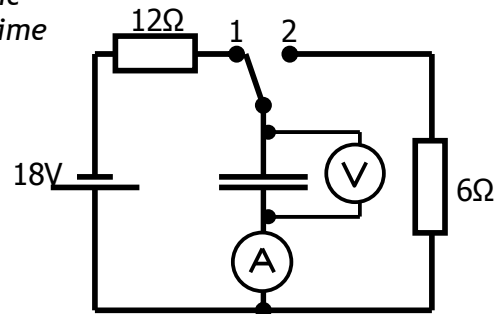

## Tutorial 7 Capacitors 2 (extension problem solving)

1. State three common uses for a capacitor in small electrical devices. Describe how it is used in each case.

Camera - store energy for quick release in flash

Tuning - Filter out low or high frequency

Time delay lights (interior in cars) - keeps lights on for a few seconds after power supply is removed

2. A  $400\text{nF}$  capacitor is allowed to fully charge to  $9\text{V}$ .

(a)  $1.62 \times 10^{-5} \text{ J}$

(b)  $6.63 \text{ V}$


3. To produce the correct level of brightness a camera flash must produce  $0.04\text{J}$  of energy. The flash is powered from a  $150\mu\text{F}$  capacitor. To what voltage must the capacitor charge in order to provide this much energy?

$23 \text{ V}$

4. At a point during charging the voltmeter reads  $3\text{V}$  in the circuit shown. Calculate:

(a)  $0.012 \text{ A}$

(b)  $5.4 \times 10^{-3} \text{ C}$

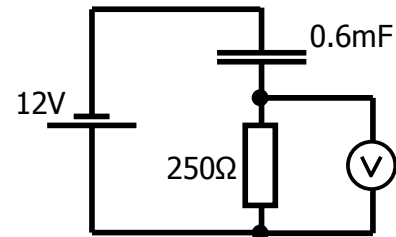


5. A capacitor is charged by a constant current of  $20\mu\text{A}$  for 12 seconds and reaches a voltage of  $12\text{V}$ . Calculate

(a)  $Q=It=2.4 \times 10^{-4} \text{ C}$




(b)  $20 \mu\text{F}$

- 6.

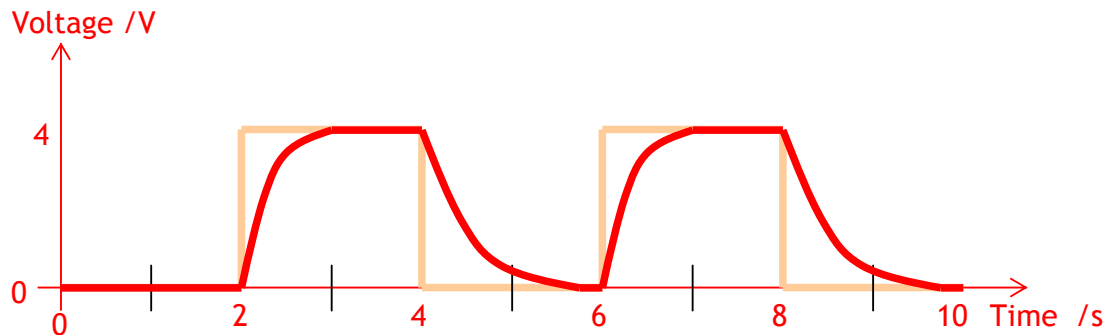


## Tutorial 8 Inverting Mode Op-Amps

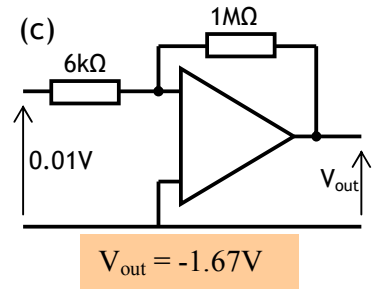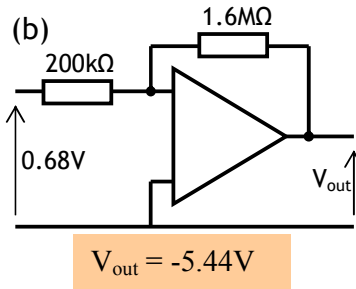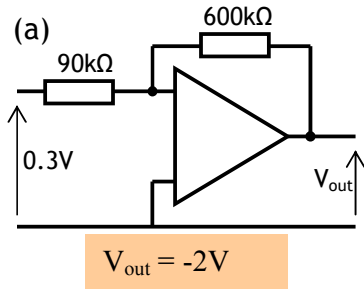1. For each of the following, calculate the voltage output. Assume that no amplifiers in this question reach saturation.





2. Adjusting the value of the variable resistor in the following circuit will alter the gain of the operational amplifier, which has a saturation voltage of  $\pm 13V$ . At what value of resistance will the output voltage of the amplifier become saturated?

$R_f = 1.625 \text{ M}\Omega$

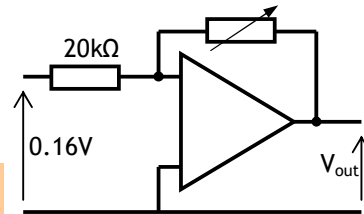

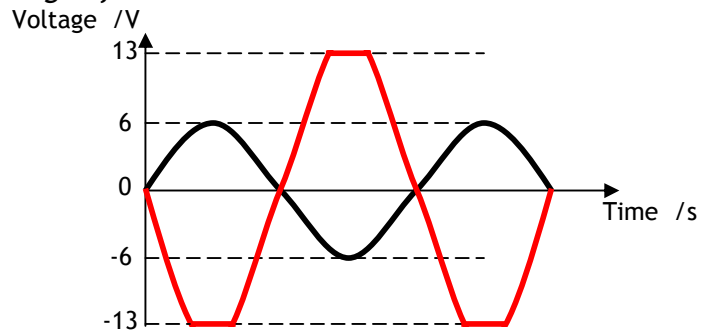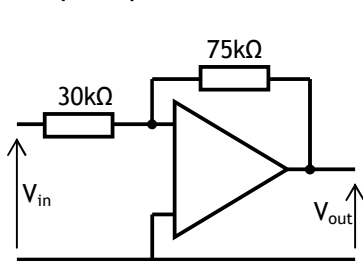3. The following AC input voltage is applied to the op-amp as shown. Neatly sketch a copy of this graph then add a second line to show how the output voltage varies with time. Numerical values should be included on the voltage axis. Assume that the op-amp saturates at a voltage of  $\pm 13V$ .



4. An op-amp is required to produce an output of 9.6volts from an input of -0.52V. The saturation voltage of the op-amp is  $\pm 12V$ .  
 (a) Suggest a combination of feedback and input resistors which would fulfil this requirement.

Any combination of resistors such that  $R_f/R_1=18.46$





- (b) At what input voltage will the op-amp output voltage become saturated?

$V_{in}=0.65V$

# Tutorial 9

## Differential Mode Op-Amps

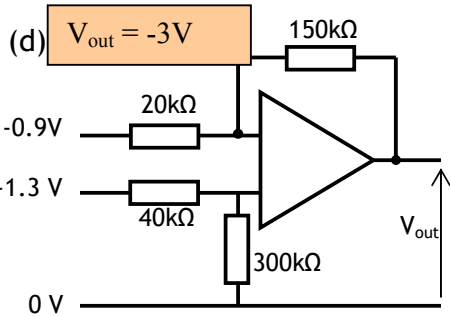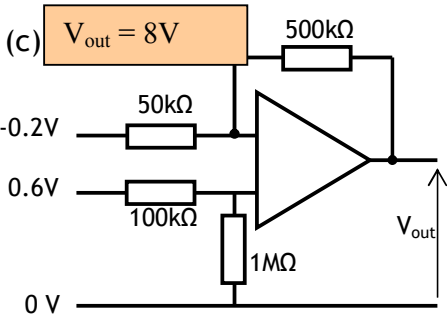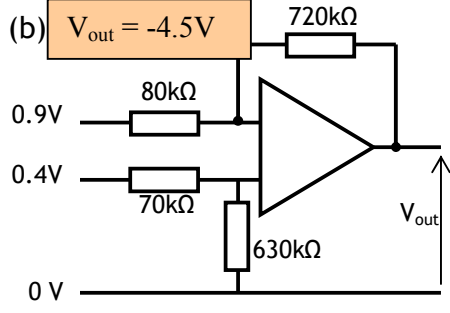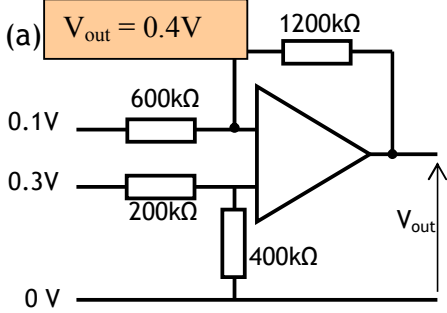
1. Find the output voltage in each of the following differential mode op-amps.



2. An operational amplifier is set up in differential mode fitted with  $500\text{k}\Omega$  input resistors and  $2\text{M}\Omega$  feedback resistors in their normal positions. The non inverting input has a voltage of  $0.4\text{V}$  applied to it. An unknown voltage is applied to the inverting input. The output voltage is measured to be  $1.4\text{V}$ .


- (a) Draw the circuit diagram for this op-amp including all the information given in the question.
- (b) Calculate the unknown voltage.  $V_1 = +0.05\text{V}$

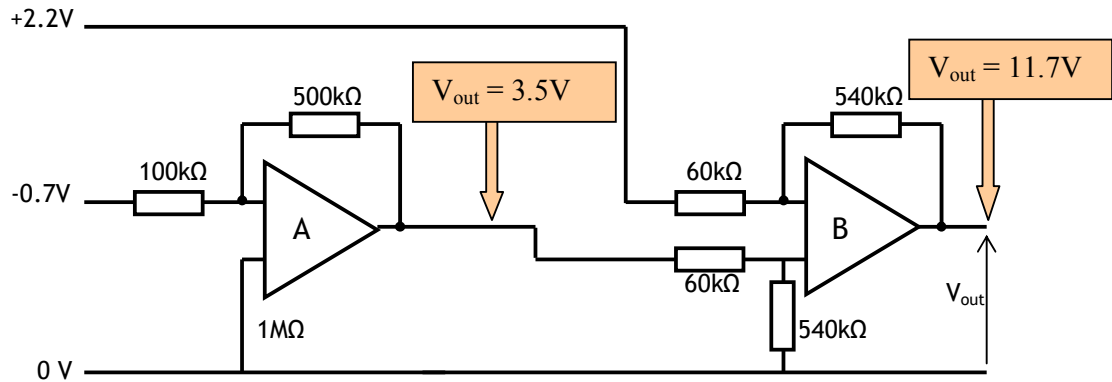3. Calculate the overall output voltage of the following circuit. Show all your working and state the output voltage after each amplifier.




## Tutorial 10 Op-Amp Control Circuits

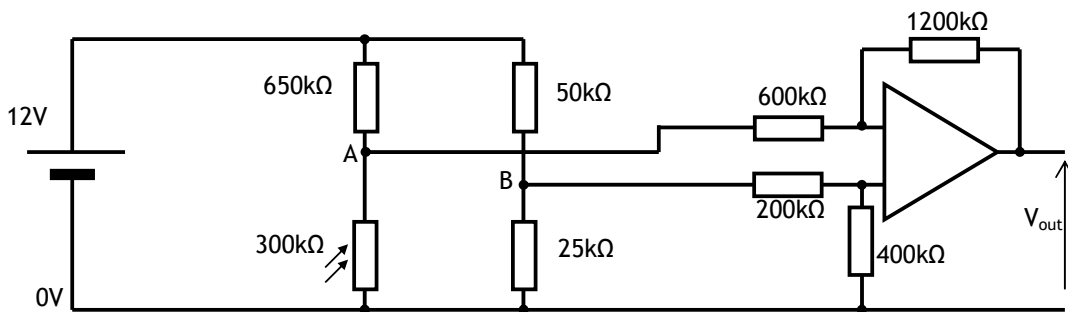1. A wheatstone bridge is setup and is connected to an operational amplifier as shown in the circuit diagram below. The saturation voltage for the op-amp is  $\pm 14\text{ V}$ . Under current conditions the LDR has a resistance of  $300\text{ k}\Omega$ .
- State the mode in which the op-amp is operating **Differential Mode**
  - Calculate the potential at point A  **$3.79\text{ V}$**
  - Calculate the potential at point B  **$4\text{ V}$**
  - Calculate the potential difference between point A and point B  **$0.21\text{ V}$**
  - Calculate the output voltage of the op-amp  **$0.42\text{ V}$**
  - If the light level changes such that the output voltage is zero, calculate the resistance of the LDR. **If  $V_{\text{out}}=0$ ,  $V_A=V_B$ ,  $R_{\text{LDR}}=325\Omega$**





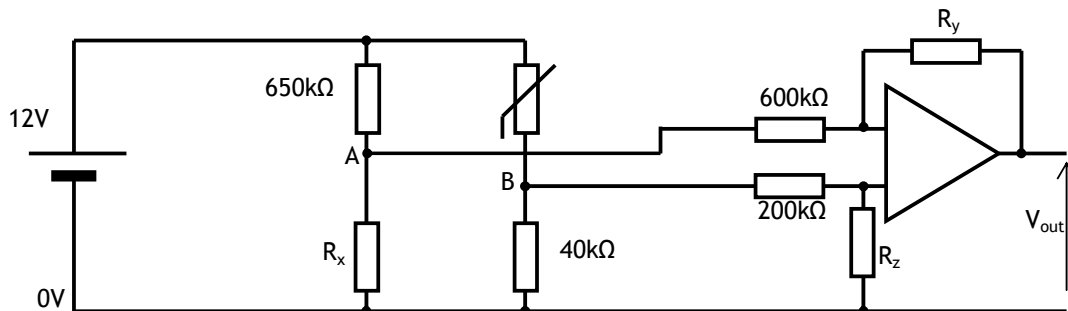2. The circuit below is to be used as a digital thermometer. As the resistance of the thermistor changes, the voltage output will also change and his reading can be converted to a temperature. In order to calibrate the system, you must choose appropriate values of resistor for  $R_x$ ,  $R_y$ , and  $R_z$ . You test the resistance of the thermistor at  $0^\circ\text{C}$  and  $100^\circ\text{C}$  and find the resistances to be  $34\text{ k}\Omega$  and  $30\text{ k}\Omega$  respectively.
- $R_x=765\Omega$**
  - $V_A=6.48\text{ V}$  ...  $V_B=6.86\text{ V}$  ...  $V_{AB}=0.37\text{ V}$**
  - $R_y=162\text{ M}\Omega$  ...  $R_z=54\text{ M}\Omega$**



## Tutorial 11 Summary

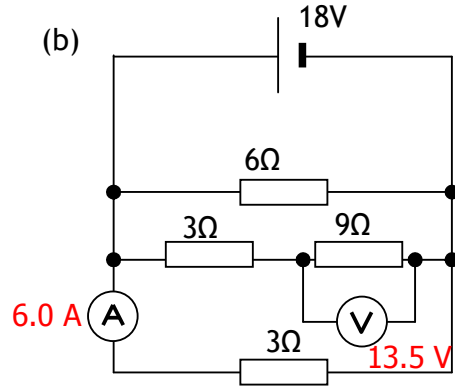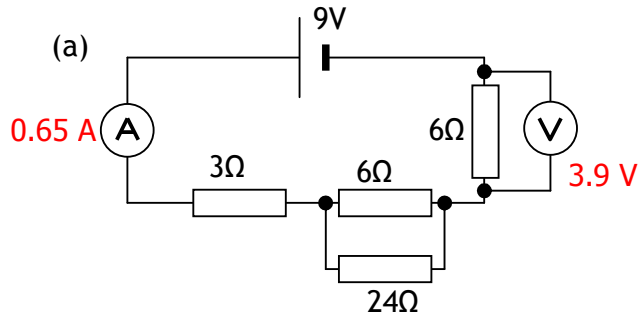1. Calculate the readings on the voltmeter and ammeter in each of the following circuits



2. An AA cell has an emf of 1.55V. Its internal resistance is 0.9Ω. The cell is connected to a heater which has a resistance of 1.1Ω. Calculate:
- 0.78 A
  - 0.86 V
  - 0.67 W
  - 73 J
  - 0.63 W
3. A 120μF capacitor is charged to 23V. It is then allowed to discharge through a 3kΩ resistor. Calculate:
- 0.032 J
  - 2.8 mC
  - 7.7mA
4. For each of the following op-amp circuits, state which mode the op-am is operating in and calculate the values of any missing voltages or resistances marked with a question mark.

